


Combinational Circuit

- A combinational circuit is a connected arrangement of logic gates with a set of inputs and outputs. To design combinational circuit following procedure is involved:
 - The problem is stated.
 - The input and output variables are assigned letter symbols.
 - The truth table that defines the relationship between inputs and outputs is derived.
 - The simplified Boolean functions for each output are obtained.
 - The logic diagram is drawn

Half Adder

A combinational circuit that performs the arithmetic addition of two bits is called a half-adder.


Input		Output	
X	Y	Sum	Carry
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

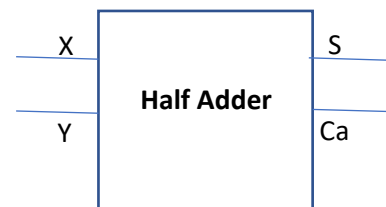

Block Diagram

Carry: $x \cdot y$

Sum: $x'y + xy'$ (or) $x \oplus y$

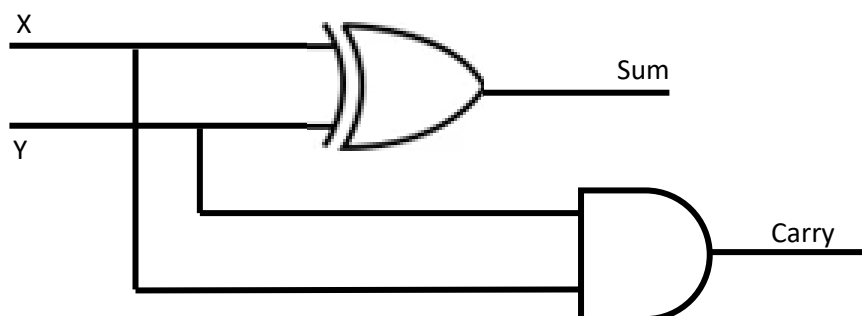

Logic Diagram

Full Adder

A full-adder is a combinational circuit that forms the arithmetic sum of three input bits

Number of inputs: 3 Number of Output: 2

Carry : $x \cdot y + (x \oplus y)z$

Sum: $x \oplus y \oplus z$



Block Diagram

Truth Table:

Inputs			Outputs	
X	Y	Z	CARRY	SUM
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{Carry} = x'yz + xy'z + xyz' + xyz$$


$$= z(x'y + xy') + xy(z' + z)$$

$$= z(x \oplus y) + xy$$

$$\text{Sum} = x'y'z + x'yz' + xy'z' + xyz$$

$$= x'(y'z + yz') + x(y'z' + yz)$$

$$= x \oplus y \oplus z$$

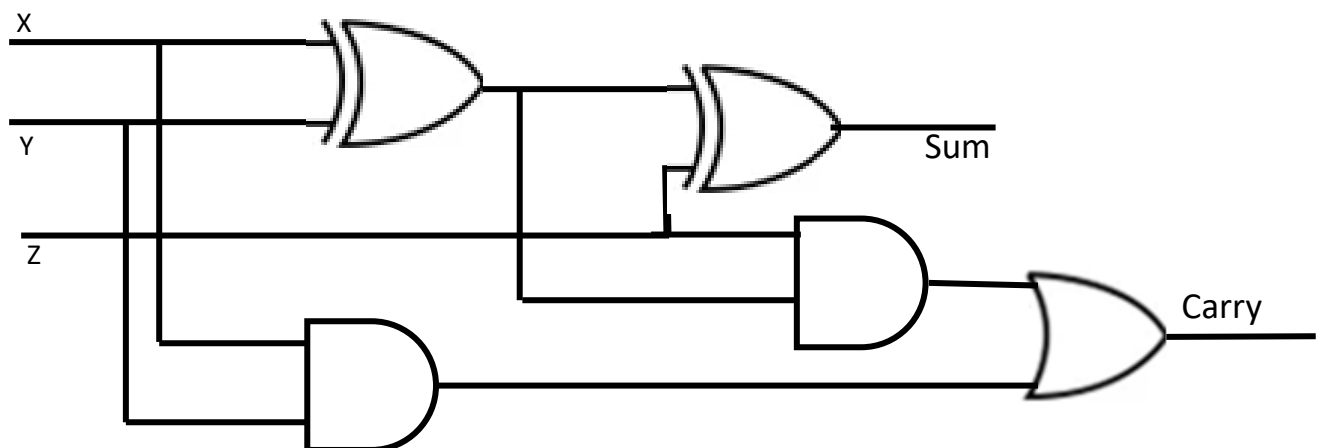

Logic Diagram


Half Subtractor

The half subtractor is a combinational circuit which is used to perform subtraction of two bits. [X:Minuend; Y:Subtrahend]

Difference: $x \oplus y$

Borrow: $x' \cdot y$

Input		Output	
X	Y	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

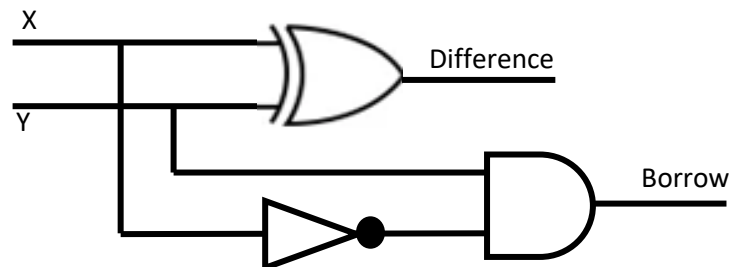

Logic Diagram

Full Subtractor

A full subtractor is a **combinational circuit** that performs subtraction of two bits, one is minuend and other is subtrahend, considering borrow of the previous adjacent lower minuend bit. This circuit **has three inputs and two outputs**. The three inputs A, B and Bin, denote the minuend, subtrahend, and previous borrow, respectively. The two outputs, D and Bout represent the difference and output borrow, respectively.

Inputs		Outputs		
X	Y	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Difference} = x'y' B_{in} + x'y B_{in}' + xy' B_{in}' + xy B_{in}$$


$$\text{Difference} = x'(y' B_{in} + y B_{in}') + x(y' B_{in}' + y B_{in})$$

$$\text{Difference} = x \oplus y \oplus B_{in}$$

$$\text{Borrow} = x'y' B_{in} + x'y B_{in}' + x'y B_{in} + xy B_{in}$$

$$\text{Borrow} = B_{in} (x'y' + xy) + x'y(B_{in}' + B_{in})$$
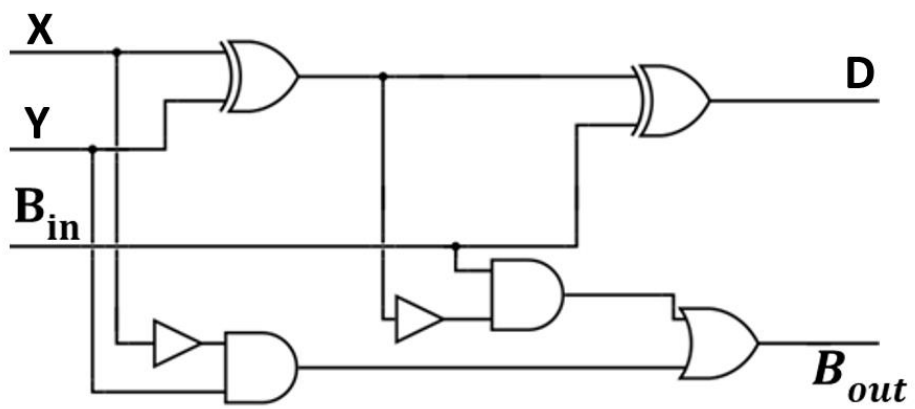
$$\text{Borrow} = B_{in} (x \oplus y)' + x'y$$



Logic Diagram